

EEE3096 tut 4

Learning Objective

DAC Metrics

1.

$$V_{out} = K \cdot Digitalin$$

$$10m = K \cdot 20$$

$$K = 0.5 \cdot 10^{-3}$$

$$\therefore V_{out} = K \cdot Digitalin$$

$$\therefore V_{out} = 14.5 mV$$

$$2. \quad K = \frac{Full\ Scale\ Value}{Max\ digital\ input} = \frac{10m}{2^{12}-1} = 2.442 \cdot 10^{-6}$$

$$V_{out\ target} = (K \cdot Digitalin)$$

$$V_{out\ target} = (2.442 \cdot 10^{-6} \cdot (2048))$$

$$5.001 mV$$

$$Full\ scale\ error = 0.5\% \cdot 10mV = 0.05mV$$

$$\therefore V_{out} = 4.951\ to\ 5.051 [4.951, 5.051]$$

DAC Design

$$1. \quad Resolution_{bits} = \log_2 \left(\frac{F_{clk}}{F_{pwm}} \right) \text{ (I fixed the formula using log rules)}$$

$$F_{pwm} = \frac{F_{clk}}{2^{bit\ resolution}}$$

$$F_{pwm\ max} = \frac{72Mhz}{2^{10}} = 70.3\ kHz$$

$$2. \quad (ARR + 1)(PSC + 1) = \frac{F_{clk}}{F_{pwn}} = 2^{resolution} = 2^{10} = 1024$$

$$\text{So choose } ARR = PSC = 31, \text{ thus } (31 + 1) \cdot (31 + 1) = 1024$$


3. Calculations

$$f_c = 5kHz = \frac{1}{2\pi RC}$$


Choose $C = 10nF$

$$\therefore R = \frac{1}{2\pi \cdot 5kHz \cdot 10nF} = 3.183 k\Omega$$


The circuit design.

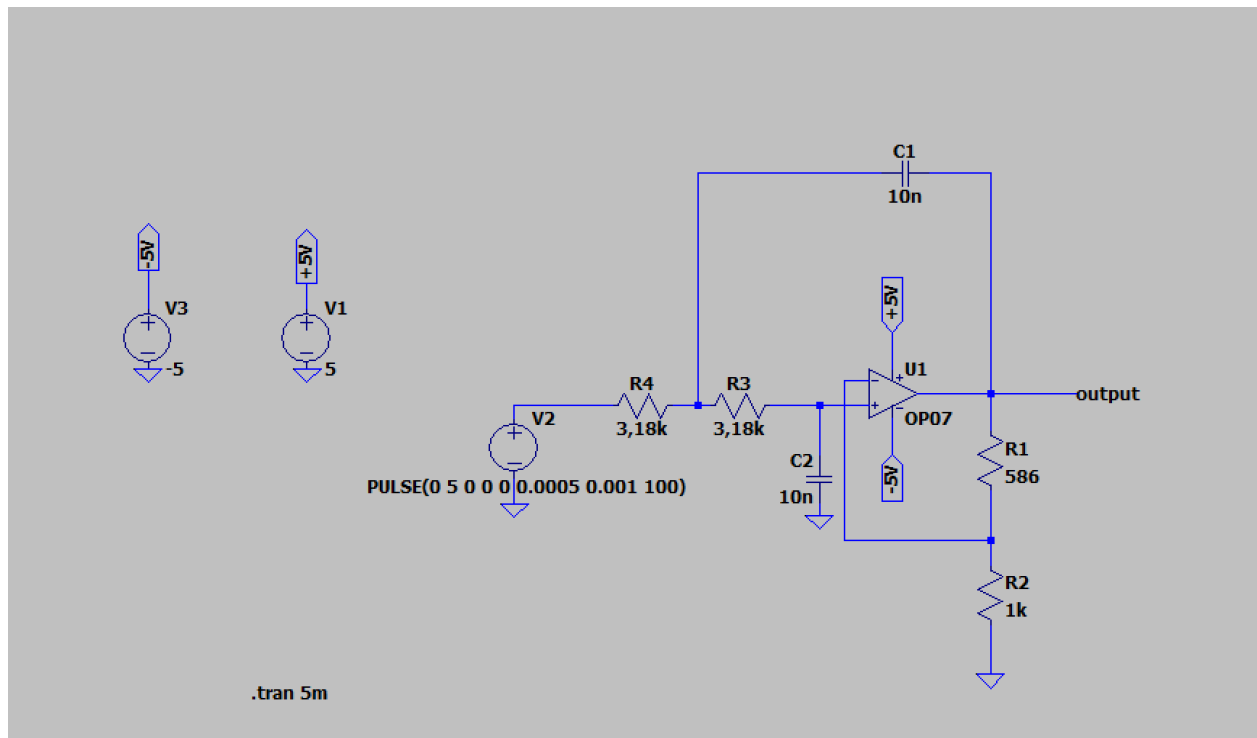


Result at 1KHz:

 

Result at 5KHz:

 

Result at 20 KHz:

 

All test so far have been done at 50% duty cycle

This is at a lower duty cycle.

